

(a) Maximum value of  $v_o$  is 0V. ~~No. of one~~

(b) VRIPPLE =  $< 1V$

$$\Rightarrow \frac{|\min(v_s) + V_F|}{2FRC} < 1V$$

$$\Rightarrow \frac{11.3}{120 \times 10 \times C} < 1$$


$$\Rightarrow C > \frac{11.3}{1200} F$$

$$PIV \text{ rating} = 2 \max(v_s) - V_F = 23.3V$$

$$\begin{aligned} v_s^{\text{rms}} &= 8.5V \\ \min(v_s) &= -\sqrt{2} \times 8.5V \\ &\approx 12V \end{aligned}$$

2.9

(2)

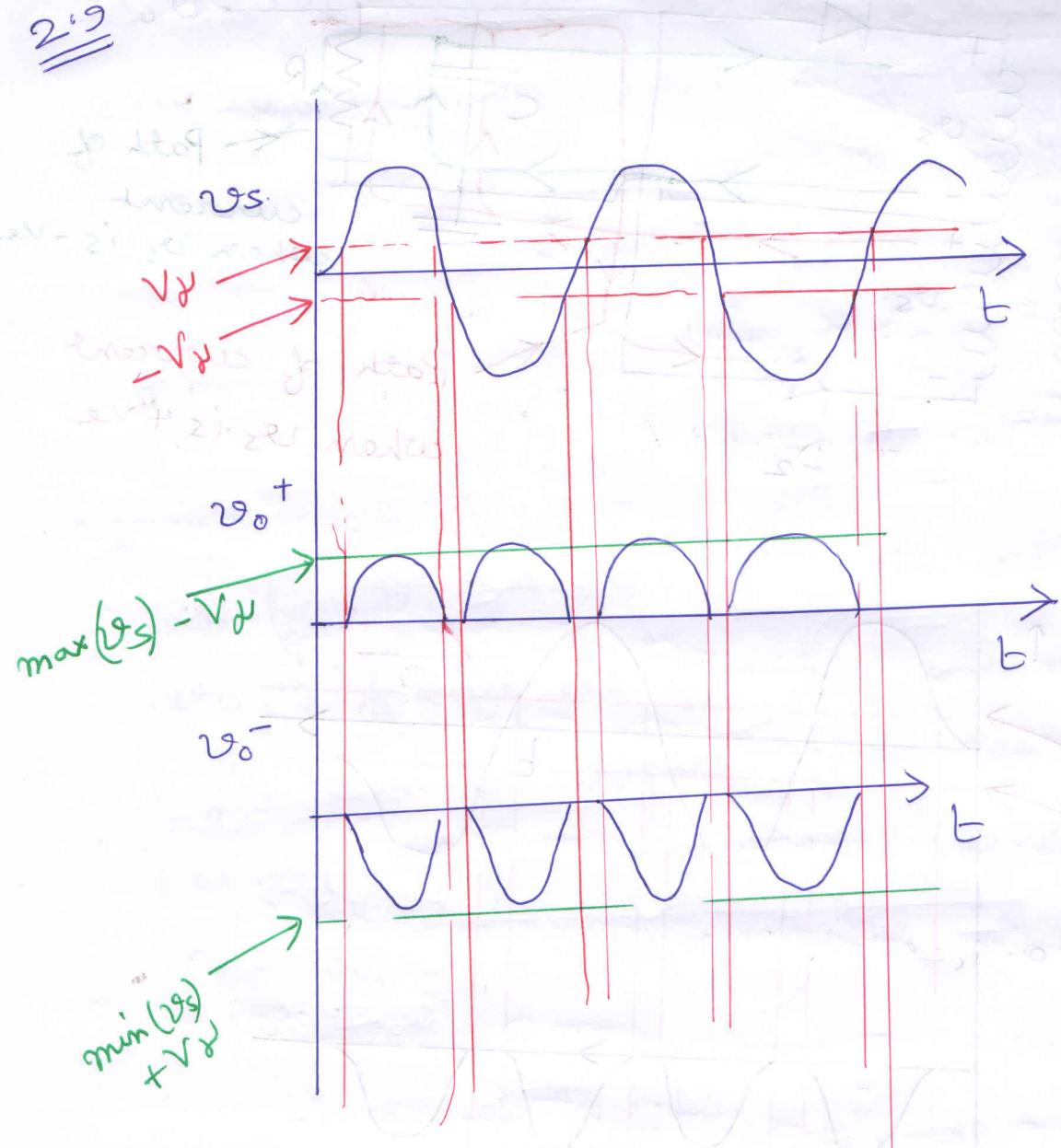

$$\sqrt{2 \cdot 8} = 4\sqrt{2}$$

$$(4\sqrt{2}) \text{ V rms}$$


$$4\sqrt{2} \times \sqrt{2} = 16$$

$$16 \text{ V rms}$$


$$V_{0.88} = 4V - (2t) \cos \theta = 4t \sin \theta = 4t \cdot \frac{\sqrt{3}}{2} = 2\sqrt{3}t$$

2.12

(3)

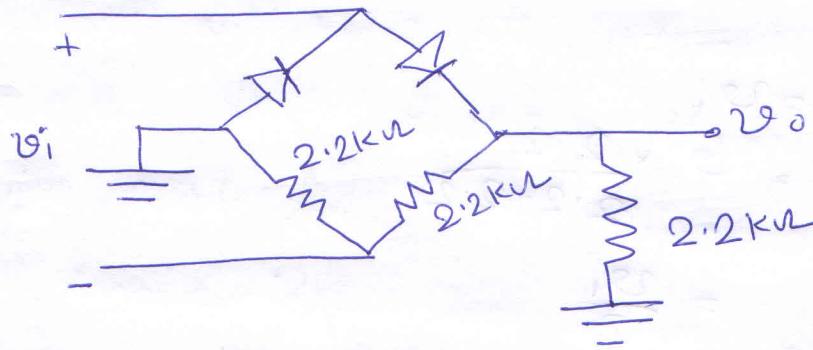

Equivalent circuit:

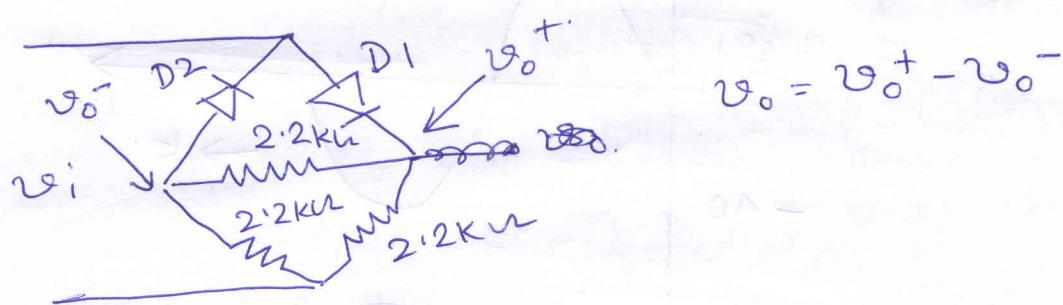

Resistance faced by current path during forward bias  
(positive half cycle)

$$\text{forward bias}_N = (2.2 \text{ k}\Omega + 2.2 \text{ k}\Omega) \parallel 2.2 \text{ k}\Omega$$

$$= 4.4 \text{ k}\Omega \parallel 2.2 \text{ k}\Omega$$

$$= \frac{2}{3} \times 2.2 \text{ k}\Omega$$

$v_o^+ = v_o^-$  For  $v_i > 0$ ,

$$v_o^+ = v_i$$

$$v_o^- = v_i \times \frac{2.2}{2.2 + 2.2}$$

$$= \frac{v_i}{2}$$

$$\text{So, } v_o = v_o^+ - v_o^- = \frac{v_i}{2}$$

3½


During ~~reverse bias~~ negative half cycle D2 is activated.

$$v_0^- = v_i$$

$$v_0^+ = v_i \times \frac{2 \cdot 2}{2 \cdot 2 + 2 \cdot 2}$$

$$= \frac{v_i}{2}$$
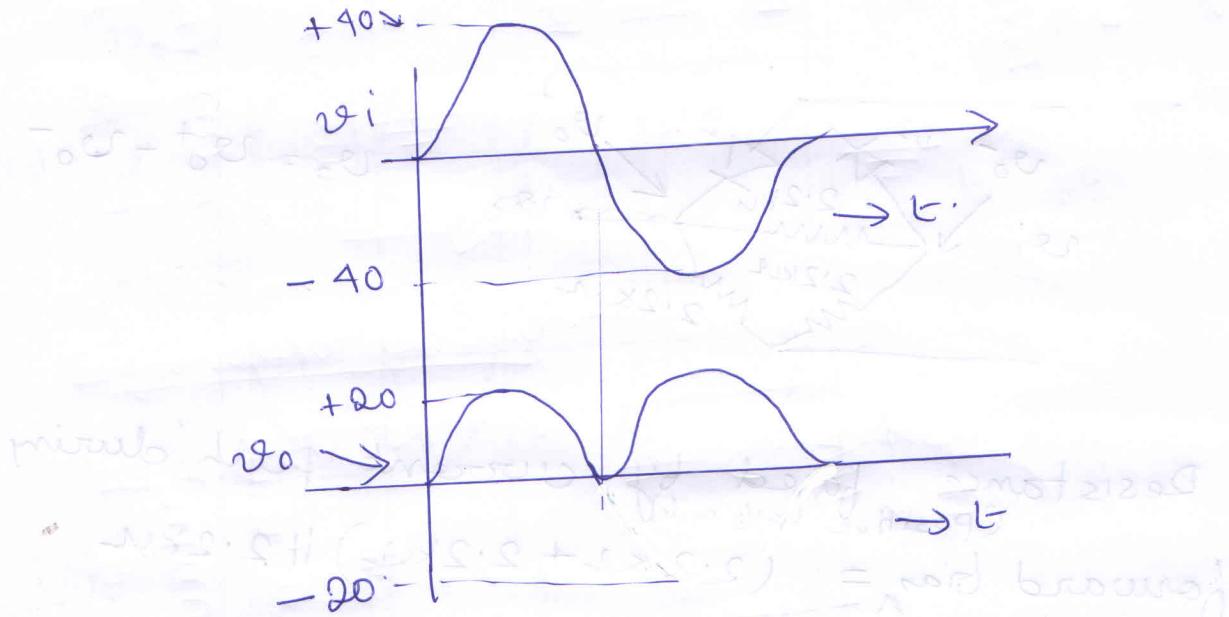
$$\text{So, } v_0 = v_0^+ - v_0^- = -\frac{v_i}{2}$$



RMS value is independent of the polarity of each half cycle.

$$\text{So, } v_o^{\text{rms}} = \frac{\max(v_o)}{\sqrt{2}}$$

$$= \frac{20}{\sqrt{2}}$$

$$= 14.14 V$$

2.2)

(a). Minimum Zener

diode current is 5mA.

~~so~~, The load current

may vary from 0 to 20mA. So, to

maintain regulation  $R_i$  must be able to pass  $i_z^{\min} + i_L^{\max}$  at  $V_{ps}^{\text{mix}}$ . So, the

value of  $R_i$  must be.


$$R_i = \frac{V_{ps}^{\min} - V_2}{i_z^{\min} + i_L^{\max}} \quad V_{ps}^{\min} = 20V - 25 \times 20V \\ = 15V$$

$$\approx \frac{15V - 10V}{5mA + 20mA} \quad (\text{Assume } V_2 \approx 10V)$$

$$\approx \frac{5V}{25mA}$$

$$\approx 200\Omega$$

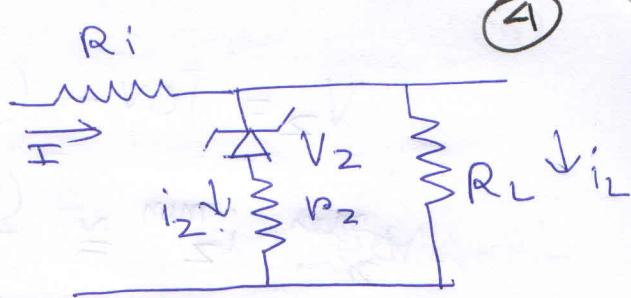(b) The output voltage is minimum when  $i_z$  is minimum and maximum when  $i_z$  is maximum (due to the presence of  $r_z$ ).  $i_z$  is minimum when  $V_{ps}$  is maximum and  $i_L$  is maximum.  $i_z$  is minimum and  $i_L$  is maximum when  $V_{ps}$  is minimum and  $i_L$  is minimum.



$$V_2 = 10V + (i_2 - 0.025) \times 5$$

$$V_2^{\max} i_2^{\min} = \frac{(15-10)V}{200\mu\text{A}} - i_L^{\max}$$

$$\approx 25\text{mA} - 20\text{mA}$$

$$= 5\text{mA}$$

$$i_2^{\max} = \frac{V_{PS}^{\max} - V_2^{\min}}{200\mu\text{A}} - i_2^{\min}$$

$$\approx \frac{25V - 10V}{200\mu\text{A}} - 0$$

$$V_2^{\max} - V_2^{\min} \approx 75\text{mA}$$

$$(V_2^{\max} - V_2^{\min}) = (i_2^{\max} - i_2^{\min}) \times R_2$$

$$\approx (75 - 5)\text{mA} \times 5\mu\text{A}$$

$$= 0.070\text{A} \times 5\mu\text{A}$$

$$= 0.35\text{mW}$$

$$\text{Percent regulation} = \frac{V_2^{\max} - V_2^{\min}}{V_2^{\min}} \times 100\%$$

$$\approx \frac{35V}{10V} \times 100\%$$

$$\approx 350\%$$

$$2.22$$

$V_S = 24V$  at output with no load  
 $V_D = 0V$  at ground with a  
 $r_2 = 16V$

$$I_L^{\min} = 40mA \quad I_L^{\max} = 400mA$$

$$r_2 = 2\Omega$$

$$I_Z^{\min} = 40mA$$

$I_Z$  is minimum when  $I_L$  is maximum.

For proper voltage regulation,  $r_i$  must be such that it can pass  $I_L^{\max}$  while still maintaining breakdown, that is,

providing  $I_Z^{\min}$ .

$$\text{So, } r_i \approx \frac{V_S - V_Z}{I_L^{\max} + I_Z^{\min}}$$


$$= 25 \frac{24 - 16}{400 + 40} \text{ k}\Omega$$

$$= \frac{8}{440} \text{ k}\Omega = 0.01818 \text{ k}\Omega$$


$$= \frac{1}{505} \text{ k}\Omega.$$

This is the <sup>maximum</sup> value of  $r_i$ .  
 $r_2$  can be used for more accuracy.

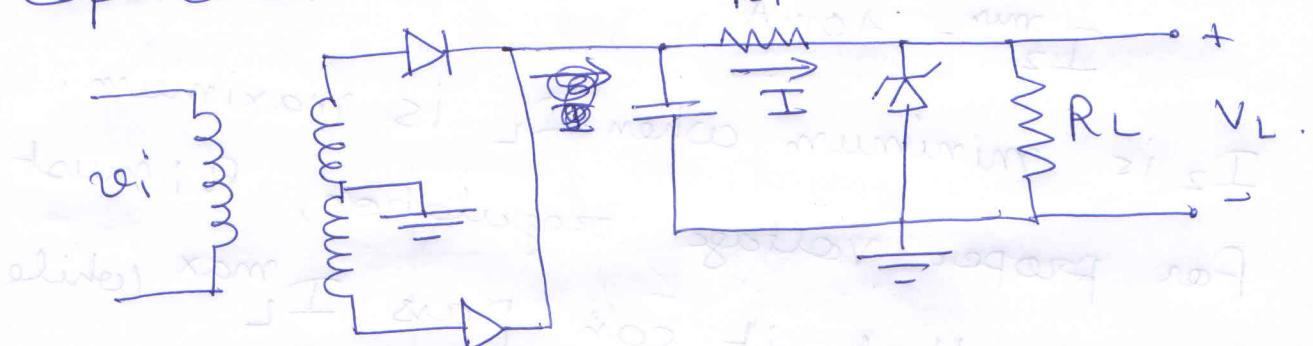Finding the ripple voltage in this case is a little tricky. To find the value of  $C_0$ , we will replace the entire part of the circuit to the left of the capacitor with an equivalent resistor  $R_i$ .



Equivalent circuit:-

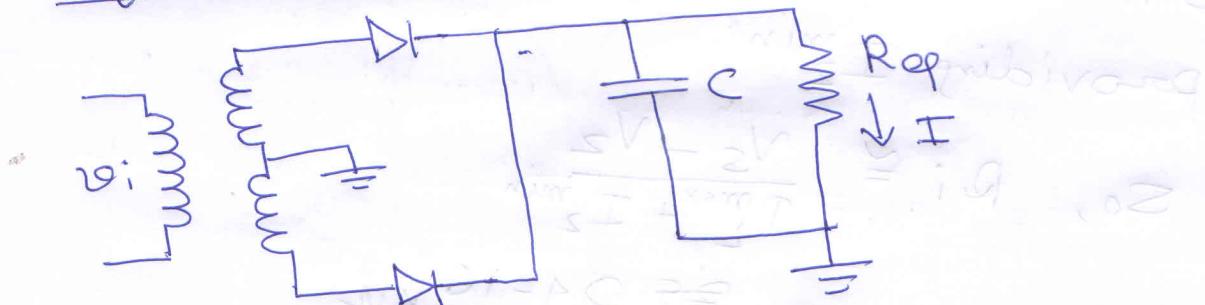

$$R_{eq} = \frac{V_s}{I} = \frac{24V}{440mA} \approx 0.0545k\Omega = 54.5\Omega$$

$$V_{RIPPLE} = \frac{V_s}{2fR_{eq}C} \leq 1V$$

Assume that  $f = 60Hz$  (frequency of ac ~~current~~ voltage in India).

$$\therefore \frac{24}{2 \times 60 \times 54.5 \times C} \leq 1$$


$$\Rightarrow C \geq \frac{24}{2 \times 60 \times 54.5} F = 0.003F$$

2.27

(8)

$$V_{out} \begin{cases} \cong V_{in} - 4.3V & \text{for } V_{in} \leq 4.3V \\ = 0 & \text{for } V_{in} > 4.3V \end{cases}$$

4.3V

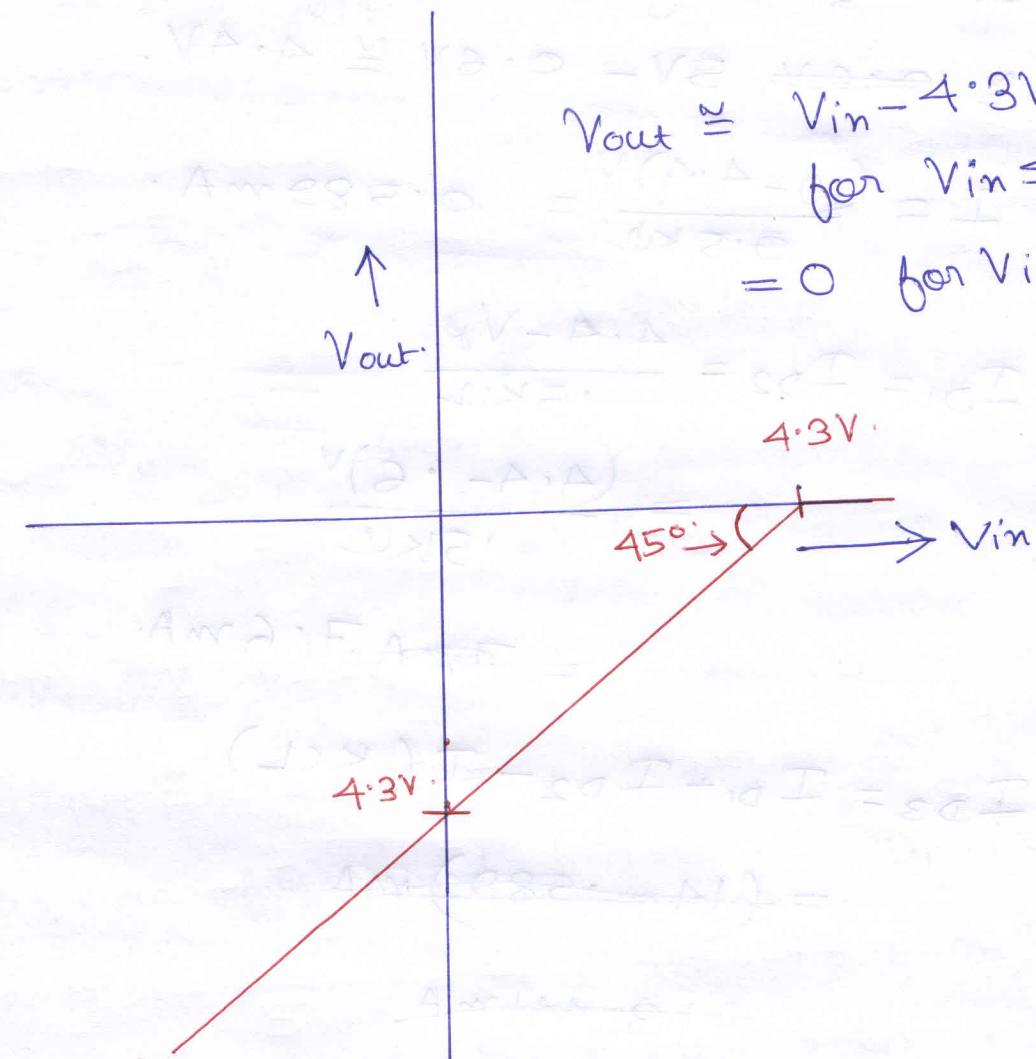

2.39  $V_F = 0.6V$   $r_p \approx 0$

(a)  $V_1 = 0$ ,  $V_2 = 0V$

The diode  $D_3$  will be forward biased.

(One way to understand this is to

assume that  $D_3$  is reverse biased and calculate  $V_o$ . If  $V_o$  is greater than  $+5V$ , then  $D_3$  is indeed reverse biased, else it is forward biased)

Since  $D_3$  is forward biased,

$$V_o \approx 0.6V. 5V - 0.6V \approx 4.4V.$$

$$I = \frac{(10 - 4.4)V}{9.5k\Omega} = 0.589mA.$$

$$I_{D1} = I_{D2} = \frac{4.4 - V_D}{5k\Omega}$$

$$= \frac{(4.4 - 0.6)V}{5k\Omega}$$

$$= 0.76mA.$$

$$I_{D3} = I_{D1} + I_{D2} - I(KCL)$$

$$= (14 - 0.589)mA$$

$$\approx 13.41mA$$

$$= (7.6 \times 2 - 0.589)mA$$

$$\approx 14.6mA$$

(b)  $V_1 = V_2 = 5V$

$D_3$  is now reverse biased.

So,  $I_{D3} \approx 0$ ,

$I_{DD} = I_{D2}$

$$I = 2I_{D1} + I_{D2} = 2I_{D1} = 2I_{D2}$$

$$= \frac{10 - 5 - V_D}{9.5k\Omega + (0.511.5)k\Omega}$$

$$= \frac{4.4V}{9.75k\Omega}$$

$$= 0.451mA$$

$$I_{D1} = I_{D2} = \frac{0.451mA}{2}$$

$$= 0.225mA$$

$$V_o = (0.225 \times 5)V + 5V - V_P$$

$$\approx 5.712V$$

(c)  $V_1 = 5V, V_2 = 0V$

Here  $D_1$  is reverse biased.  $D_2$  and  $D_3$  are forward biased.  $D_1$  is reverse biased because  $V_o$  can never be greater than  $5V - V_P = 5V - 4.4V$ .

$$So, I_{D1} = 0$$

$$V_o = 5V - V_P = 4.4V$$

$$I = \frac{10V - 4.4V}{9.5k\Omega} = 0.589mA$$

$$I_{D2} = \frac{4.4V - V_P}{9.5k\Omega} = 7.6mA$$

$$So, I_{D3} \approx I_{D2} - I_{D1} \quad (KCL \text{ with } I_{D1}=0)$$

$$= 7.01mA$$

(d) This is the reverse case of (c). Just interchange the input terminals.

~~2.3V  
d)~~

$$V_1 = 5V, V_2 = 2V, V_D = 0.7V.$$

Just check that  $V_o \neq 4.3V$ .

Just check the current.

$$I = \frac{5}{9.5} mA$$

$$I_{D1} = \frac{5 - V_D}{5}$$

$$I = \frac{10 - 4.3}{9.5} mA = \frac{5.7}{9.5} mA = \frac{57}{95} mA.$$

~~$I_{D1} = \frac{5 - 4.3}{5} mA = \frac{7}{5} mA.$~~

$$I_{D2} = I_{D1} = 0$$

$$I_{D2} = \frac{4.3 - 2 - V_D}{5} mA$$

$$= \frac{1.7}{5} mA$$

$$> \frac{17}{5} mA$$

$$\text{So, } I_{D1} + I_{D2} > I$$

or equal to.

Hence  $V_o$  must be less than  $4.3V$ .

So, that  $D_3$  is forward biased.

$D_1$  is always reverse biased.

So, Since  $D_3$  is a diode,

$$V_o = 5V - V_D = 4.3V$$

2.41

12

For  $v_i < V_F = 0.6V$ , both  $D_1$  and  $D_2$  are ~~in~~ below the cut-in voltage.

$$\text{So, } v_o = \frac{500}{5k\mu A + 5k\mu A} \times v_i = \frac{5k\mu A}{10k\mu A} v_i = \frac{v_i}{2}$$

$$V_F + 4V_D = \frac{1}{11} v_i \quad \text{hence } \frac{10}{11} v_i =$$

The drop across  $D_1$  is

$$\text{This continues till } v_i \text{ crosses } \frac{11}{10} V_F \\ = 0.66V.$$

When  $v_i$  crosses  $0.66V$ ,  $D_1$  becomes forward biased.  $D_2$  is still reverse biased.

So, The total current is to

be solved by the equation

$$I_{tot} = \frac{v_i - v_o}{5k\mu A} + \frac{v_i - v_o - V_F}{5k\mu A}$$

( $I_{tot}$  is in mA)

$$v_o = 0.5 \times I_{tot}$$

$$\text{Now, } I_{tot} = \frac{v_i - 0.5 I_{tot}}{5} + \frac{v_i - 0.5 I_{tot} - V_F}{5}$$

$$\Rightarrow 5I_{tot} = v_i - 0.5I_{tot}$$

$$\Rightarrow 5I_{tot} = v_i + 2v_i - 0.5I_{tot} - V_F$$

$$\Rightarrow 6I_{tot} = 2v_i - V_F$$

$$\Rightarrow I_{tot} = \frac{v_i}{3} - \frac{V_F}{6}$$

$$= \left( \frac{v_i}{3} - 0.1 \right) \text{mA}$$

13

$$V_o = 0.5 \times I_{\text{tot}}$$

$$= \left( \frac{v_i}{6} - 0.05 \right) V$$

This continues till  $v_o$  reaches  $0.6V$ .  
when  $D_2$  becomes forward biased and  
crosses the cut-in voltage.

When  $v_o = 0.6V$ ,  $v_i = 3.9V$ .

For  $v_i > 3.9V$ ,  $D_2$  is forward biased.

The total current is now  
solved by solving the following  
equation:-

$$I_{\text{tot}} = \frac{v_i - v_o}{5} + \frac{v_i - v_o - V_H}{5} = \frac{v_o}{0.5} + \frac{v_o - V_H}{0.5}$$

( $I_{\text{tot}}$  is in mA)

$$\Rightarrow (v_o - V_H)$$

$$\Rightarrow (v_o - 0.05 \times 5)$$

~~$$2v_i$$~~

$$\Rightarrow \frac{2v_i}{5} - \frac{V_H}{5} + \frac{V_H}{0.5} = \frac{2v_o}{0.5} + \frac{2v_o}{5}$$

$$\Rightarrow \frac{2}{5}v_i + \frac{9}{5}V_H = 4v_o + \frac{2}{5}v_o = 4.4v_o$$

$$\Rightarrow \frac{2}{5}v_i + \frac{1.8V_H}{0.2} = 4.4v_o$$

$$\Rightarrow 0.4v_i + 1.8V_H = 0.4v_o + 1.8V_H$$


$$\Rightarrow v_o = \frac{0.4v_i + 1.8V_H}{4.4}$$

$$= \cancel{28i} - \cancel{18V_R}$$

$$= \frac{4Vi + 18V_R}{44}$$


$$= \cancel{Vi} - \frac{Vi}{11} + \frac{9}{22} V_R$$

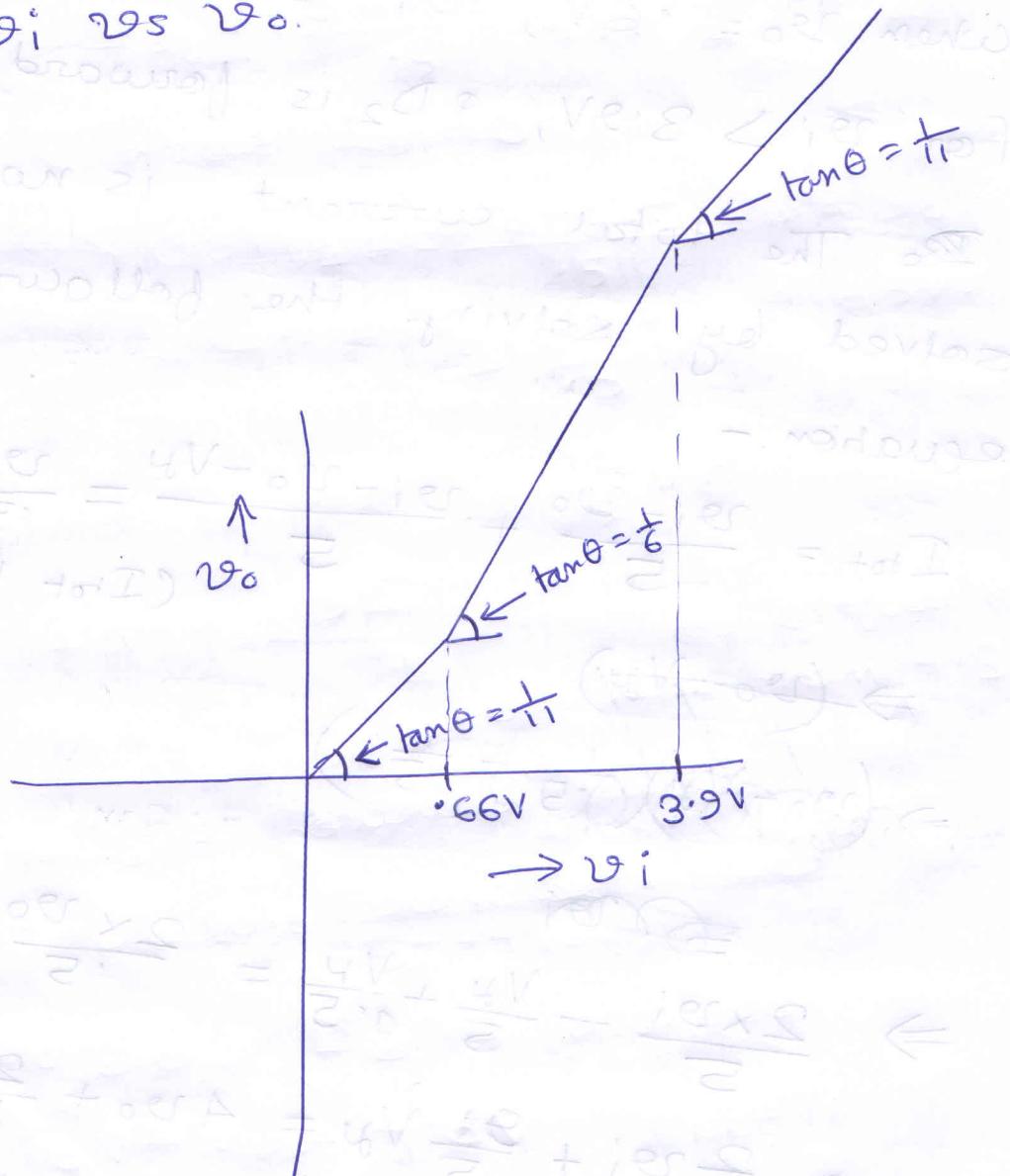Depending on the expression of  $V_o$ , for different range of  $Vi$ , you can plot  $Vi$  vs  $V_o$ .



2.42

15

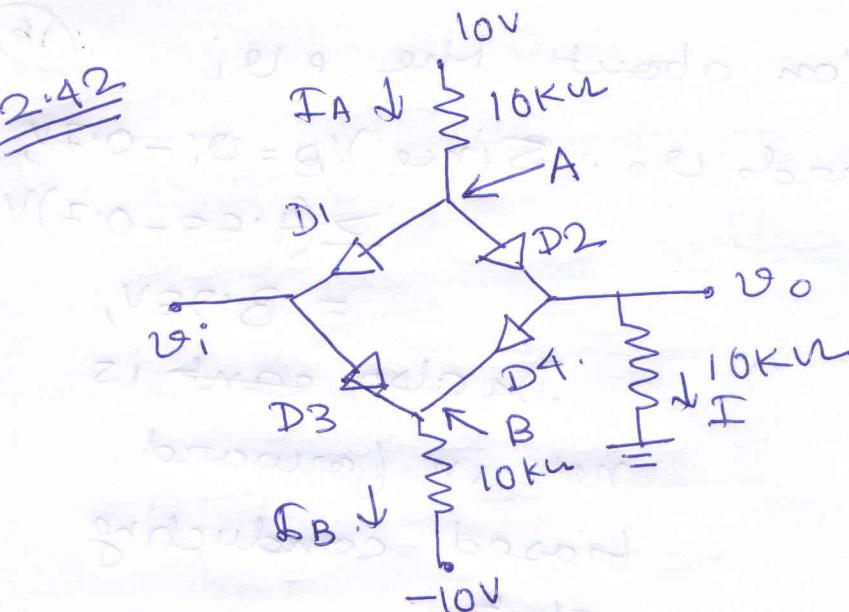

Assume  
 $v_N = -7V$ .

In the absence of the ~~now~~ input source

$v_i$ , we have  $v_o = 0$ . (Since the circuit is symmetrical.) So,  $I = 0$ .

When  $v_i$  increases from 0V,  $D_1$  immediately becomes reverse biased.

When  $v_i$  increases from 0V,  $v_A = v_i - 0.7V$ .

$v_o = v_A - v_B = v_i$ . This continues till  $I_A > I$ , so that  $I_{D1} \geq 0$ .

$$I_A = \frac{v_i - v_N}{10k\Omega} \text{ mA}, \quad I_L = \frac{v_i}{10} \text{ mA}$$

~~This~~  $v_o = v_i$  continues till  $I = I_L$ .

$$I_L = \frac{v_i}{10} \text{ mA}, \quad I_A = \frac{10 - v_i - 7}{10} \text{ mA}$$

$$\Rightarrow \frac{v_i}{10} = \frac{9.3 - v_i}{10} \Rightarrow v_i = \frac{9.3}{2} = 4.65 \text{ V}$$

When  $v_i$  increases beyond 4.65V,  $D_1$  becomes reverse biased.

So, the information about the output

$$\text{can't flow towards } v_o. \text{ Since } V_B = v_i - 0.7V, \\ \geq (4.65 - 0.7)V \\ = 3.95V,$$

$D_4$  also can't be in forward biased conducting state.

So, for  $v_i > 4.65V$ ,  $I_L = I$ . Hence

$v_o$  is fixed at  $4.65V$ . Similar

logic can be applied for  $v_i < 0$ .

For  $0 > v_i > -4.65V$ ,  $v_o = v_i$

For  $v_i < -4.65V$ ,  $v_o = -4.65V$ .

For  $v_i < -4.65V$ ,

